

Electronics Notes

Jim Emery

1/22/2011

Contents

1	Preliminaries: Resistors, Capacitors, Diodes, Transistors	3
2	October 20,2010, Oscilloscope, Oscilloscope Probe	3
3	October 27, 2010, Opamps, Feedback, Inverting Amplifier	3
4	Nov 3, 2010, Quad Opamps, Neon Bulb Firing Voltage, Inverting Amplifier, Miller Multiplication	3
5	Nov 10,2010, Building a Diode Curve Tracer, Using a Variac, an Isolation Transformer, and an Oscilloscope	3
6	Nov 17,2010 Zener diode, Opamps, Bode Plots	3
7	Dec 1, 2010, 15 volt Positive Powersupply, using the LM7805, Ideal Diode, Voltage Doubler, Buck Converter	3
8	Dec 12, 15, 2010, Operator Block Diagram of the Common Emitter,	3
9	Dec 21, 2010, LM7915 Regulator, Measuring The Frequency Response of a Common Emitter Amplifier Using the 2N3904 Transistor, The Affect of Capacitance, Solving Differential Equations With OpAmps	4

10	Jan 5, 2011, The Negative Power Supply, Using the LM7915, Switching Regulator, Harvesting Inductors for a Switching Powersupply, Measuring Inductance	4
11	Jan 12, 2011, Switching Powersupply, Measuring Transistor Parameters	4
12	Oscilloscope Probe	4
13	Using the LM7805 to Make a 15 Volt Positive Supply.	4
14	Using the LM7915 to Make a 15 Volt Negative Supply.	4
15	Measuring Inductance	5

- 1 Preliminaries: Resistors, Capacitors, Diodes, Transistors
- 2 October 20,2010, Oscilloscope, Oscilloscope Probe
- 3 October 27, 2010, Opamps, Feedback, Inverting Amplifier
- 4 Nov 3, 2010, Quad Opamps, Neon Bulb Firing Voltage, Inverting Amplifier, Miller Multiplication
- 5 Nov 10,2010, Building a Diode Curve Tracer, Using a Variac, an Isolation Transformer, and an Oscilloscope
- 6 Nov 17,2010 Zener diode, Opamps, Bode Plots
- 7 Dec 1, 2010, 15 volt Positive Powersupply, using the LM7805, Ideal Diode, Voltage Doubler, Buck Converter
- 8 Dec 12, 15, 2010, Operator Block Diagram of the Common Emitter,

Controlling the gain with resistor ratios.

<http://www.stem2.org/je/amplifier.pdf>

Using the Function Generator and Oscilloscope.

- 9 Dec 21, 2010, LM7915 Regulator, Measuring The Frequency Response of a Common Emitter Amplifier Using the 2N3904 Transistor, The Affect of Capacitance, Solving Differential Equations With OpAmps**
- 10 Jan 5, 2011, The Negative Power Supply, Using the LM7915, Switching Regulator, Harvesting Inductors for a Switching Powersupply, Measuring Inductance**
- 11 Jan 12, 2011, Switching Powersupply, Measuring Transistor Parameters**
- 12 Oscilloscope Probe**
<http://www.stem2.org/je/probe.pdf>
- 13 Using the LM7805 to Make a 15 Volt Positive Supply.**
<http://www.stem2.org/je/positivesupply.pdf>
- 14 Using the LM7915 to Make a 15 Volt Negative Supply.**
<http://www.stem2.org/je/powersupply.pdf>

15 Measuring Inductance

There are several ways to measure inductance experimentally. One method uses a function generator and an oscilloscope. So suppose a function generator generates a sinusoidal voltage v_1 and has an internal resistance R . Electrical instruments are designed to have a constant internal resistance of $R = 50\Omega$. Let us connect the function generator to an inductor of inductance L . We measure the voltage across L with an oscilloscope. The inductor has impedance $Z_L = \omega Lj$. The current in the circuit is

$$i = \frac{v_1}{Z_L + R}$$

The voltage across L is

$$\begin{aligned} v_2 &= iZ_L \\ &= \frac{v_1}{Z_L + R}Z_L. \end{aligned}$$

This circuit then acts as a voltage divider. As the frequency goes to infinity, Z_L goes to infinity. So

$$\frac{Z_L}{Z_L + R} \rightarrow 1.$$

So the voltage v_2 across L goes to the input voltage v_1 . Hence as we increase the frequency of the function generator we will see the voltage v_2 reach a steady value of v_1 . On the other hand at zero frequency all the voltage is across the resistor R . If we alter the frequency until the magnitude of v_2 equals half the magnitude of v_1 , we can determine L . So suppose for frequency ω

$$|v_2| = \frac{|v_1|}{2}.$$

Then

$$\frac{|Z_L|}{|Z_L + R|} = \frac{1}{2}.$$

That is

$$\frac{\omega L}{\sqrt{(\omega L)^2 + R^2}} = \frac{1}{2}.$$

Squaring

$$\frac{(\omega L)^2}{(\omega L)^2 + R^2} = \frac{1}{4}.$$

Then

$$3(\omega L)^2 = R^2.$$

So

$$L = \frac{R}{\omega\sqrt{3}} = \frac{R}{2\pi f\sqrt{3}},$$

where f is the frequency in cycles per second.