

# Chris Wilkson's Oscilloscope Probe Notes

James Emery

10/16/2010

## Contents

<b>1 Introduction</b>	<b>1</b>
<b>2 Properties of a 10x Probe</b>	<b>1</b>

## 1 Introduction

A oscilloscope probe is a cable containing a passive or active circuit to modify the input impedance of an oscilloscope. An oscilloscope impedance consists of resistance and capacitance.

## 2 Properties of a 10x Probe

The impedance of a capacitor of capacitance  $C$ , is given by

$$\frac{1}{j\omega C} = -\frac{j}{\omega C},$$

where  $j$  is the imaginary unit, and where  $\omega$  is the angular frequency in radians per second, and which is

$$\omega = 2\pi f,$$

where  $f$  is the frequency in cycles per second.

Suppose an oscilloscope has a load impedance of a resistor  $R_1$  and a capacitor  $C_1$  connected in parallel from the input terminal to ground. Then the impedance is defined by

$$\frac{1}{Z_1} = \frac{1}{R_1} + \frac{1}{1/(j\omega C_1)} = \frac{1}{R_1}(1 + R_1 C_1 \omega j)$$

or

$$Z_1 = \frac{R_1}{R_1 C_1 \omega j + 1}.$$

The probe consists of a resistor  $R_2$  in parallel with a capacitor  $C_2$  and has impedance

$$Z_2 = \frac{R_2}{R_2 C_2 \omega j + 1}.$$

So the impedance seen from the tip of the probe is

$$Z = Z_1 + Z_2.$$

Let us take  $R_2 = 9R_1$  and  $C_2 = C_1/9$

Then

$$\begin{aligned} Z = Z_1 + Z_2 &= \frac{R_1}{R_1 C_1 \omega j + 1} + \frac{9R_1}{9R_1(C_1/9)\omega j + 1} \\ &= \frac{10R_1}{R_1 C_1 \omega j + 1}. \end{aligned}$$

This can be rewritten as

$$Z = \frac{10R_1}{10R_1(C_1/10)\omega j + 1},$$

which is equal to the impedance of a resistor  $10R_1$  in parallel with a capacitor  $C_1/10$ . So the equivalent load seen at the probe tip has the resistance multiplied by 10 and the capacitance divided by 10.

Let voltage  $V_2$  be the voltage seen at the oscilloscope input, and  $V_1$  the voltage at the probe, then

$$V_2 = V_1 \frac{Z_1}{Z_1 + Z_2}.$$

$$Z_1 + Z_2 = \frac{R_1}{R_1 C_1 \omega j + 1} + \frac{9R_1}{9R_1(C_1/9)\omega j + 1} = 10Z_1,$$

Therefore

$$V_2 = V_1 \frac{Z_1}{10Z_1} = \frac{V_1}{10}.$$

So 1 volt at the oscilloscope corresponds to 10 volts at the probe, that is 10X.